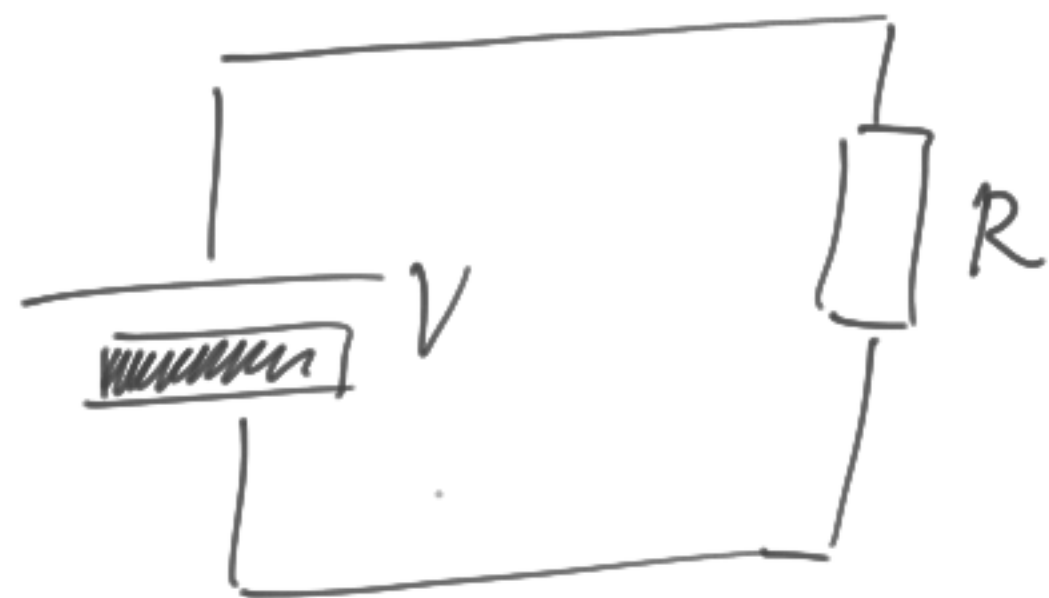


Circuit




Test 1: Find R_{eq} .

Trivial


$$V = IR$$




$$R_{eq} = R_1 + R_2 \text{ (series)}$$

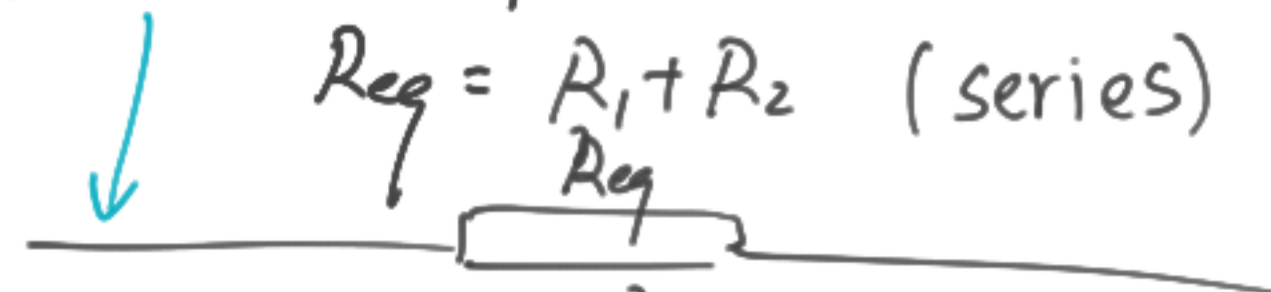
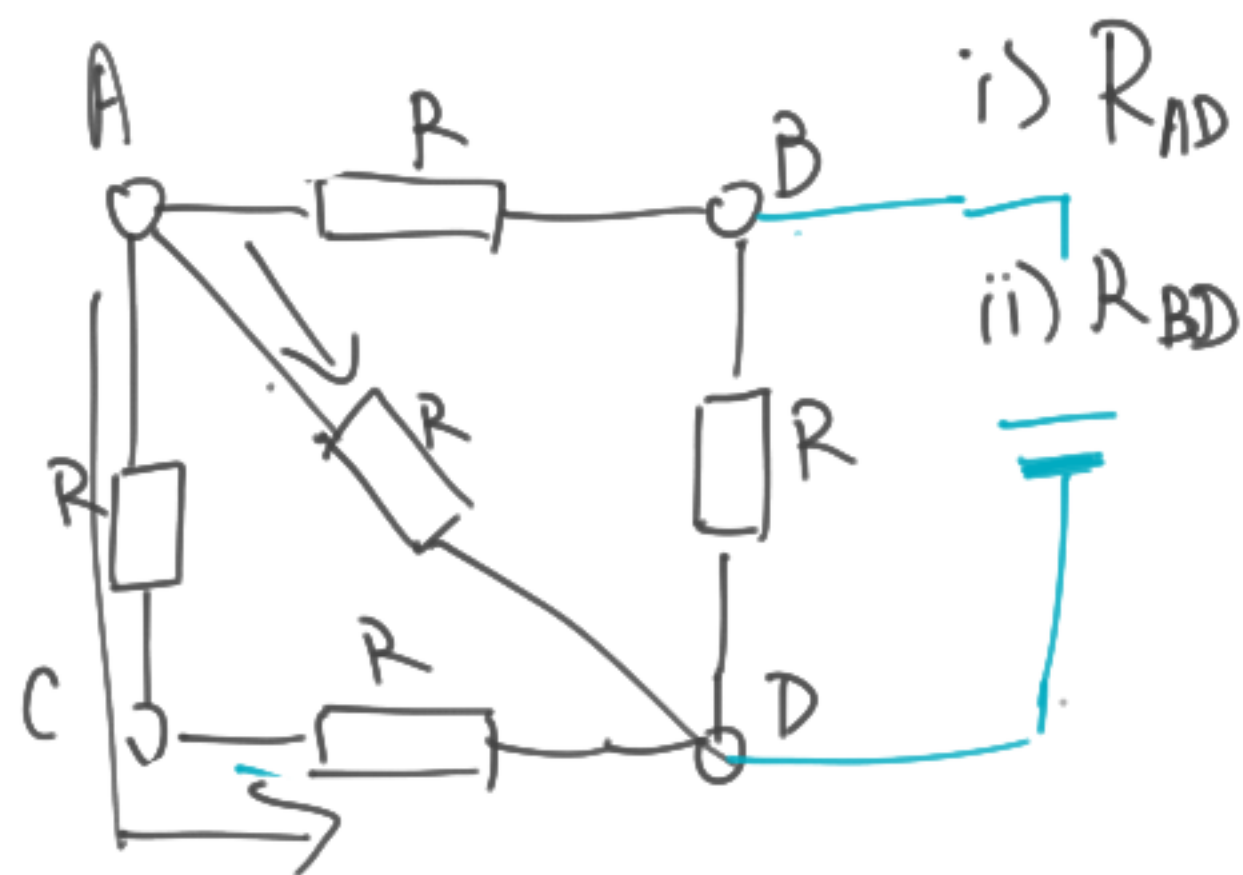
$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \text{ (parallel)}$$


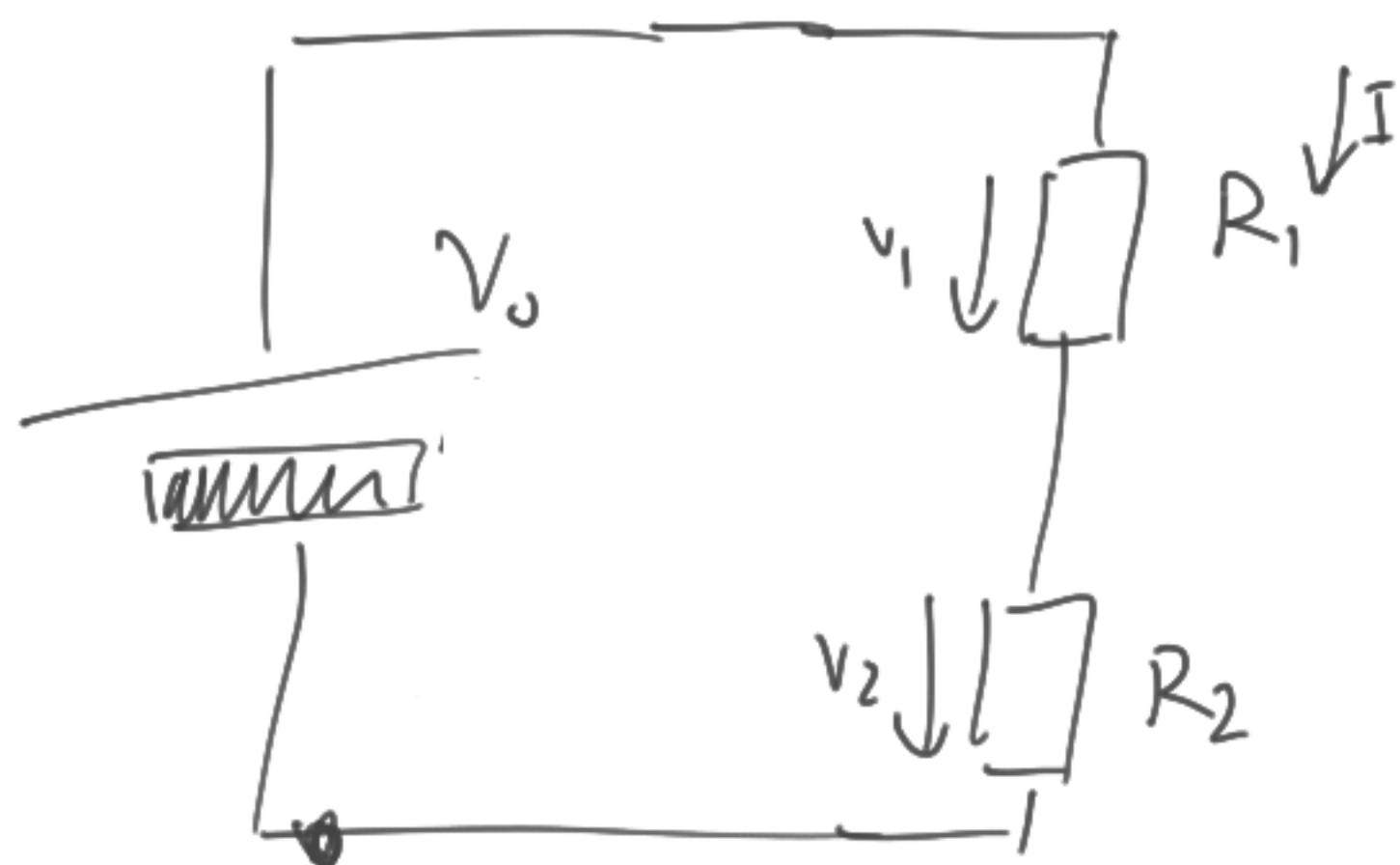
$$\begin{aligned} & \left(\frac{1}{\frac{5R}{3}} + \frac{1}{R} \right)^{-1} \\ &= \left(\frac{3}{5R} + \frac{1}{R} \right)^{-1} \\ &= \left(\frac{8}{5R} \right)^{-1} \\ &= \frac{5R}{8} \end{aligned}$$




$V_{\text{consumed}} = V_{\text{provided}}$
Things that consume V
 Resistor...

$$\therefore V = IR_1 + IR_2$$

$$V_1 + V_2 = V_0$$

Things that give V
 Battery

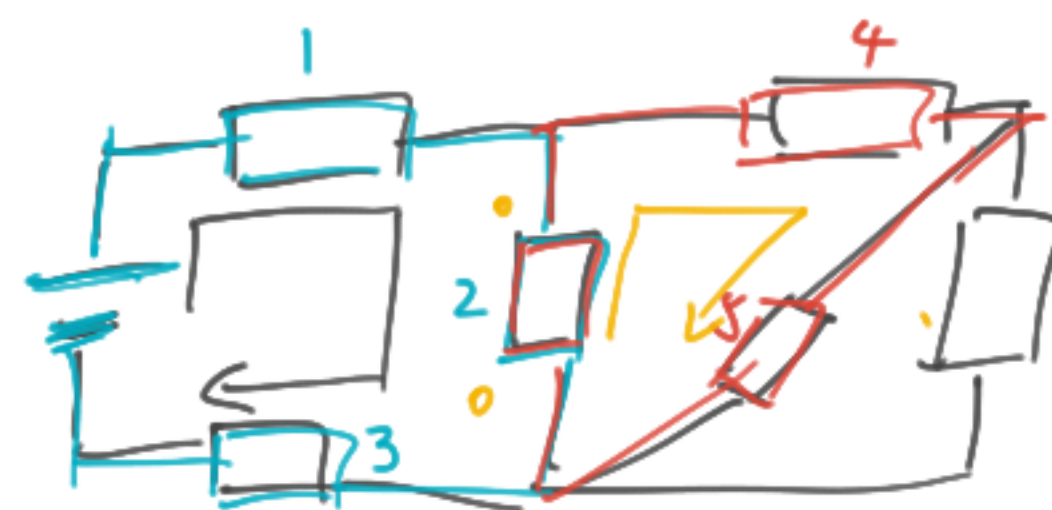

$$V = V_1 + V_2 + V_3$$

Provide


$$V_2 = V_4 + V_5$$

$$V_2 - V_4 - V_5 = 0$$

$$(2) \quad V_0 - V_3 = 0$$

$$R_3 I_2 = V_0$$

$$I_2 = \frac{V_0}{R_3}$$

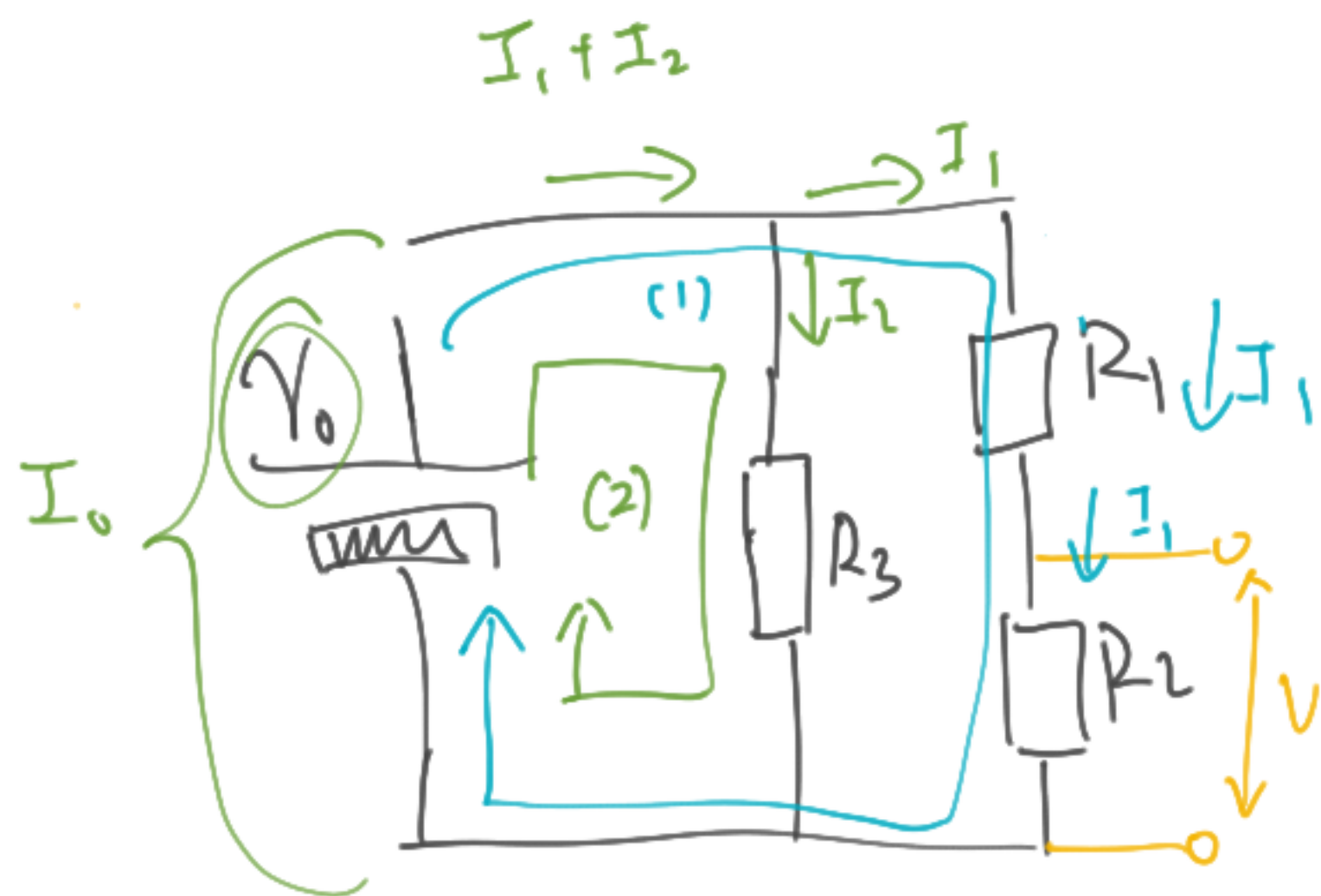


Find V across R_2 .
 in terms of V_0, R_1, R_2

$$\rightarrow V_0 - V_1 - V_2 = 0$$

$$V_0 - I_1 R_1 - I_1 R_2 = 0$$


$$I_1 = \frac{V_0}{R_1 + R_2}$$

$$V_2 = V_0 \frac{R_2}{R_1 + R_2}$$

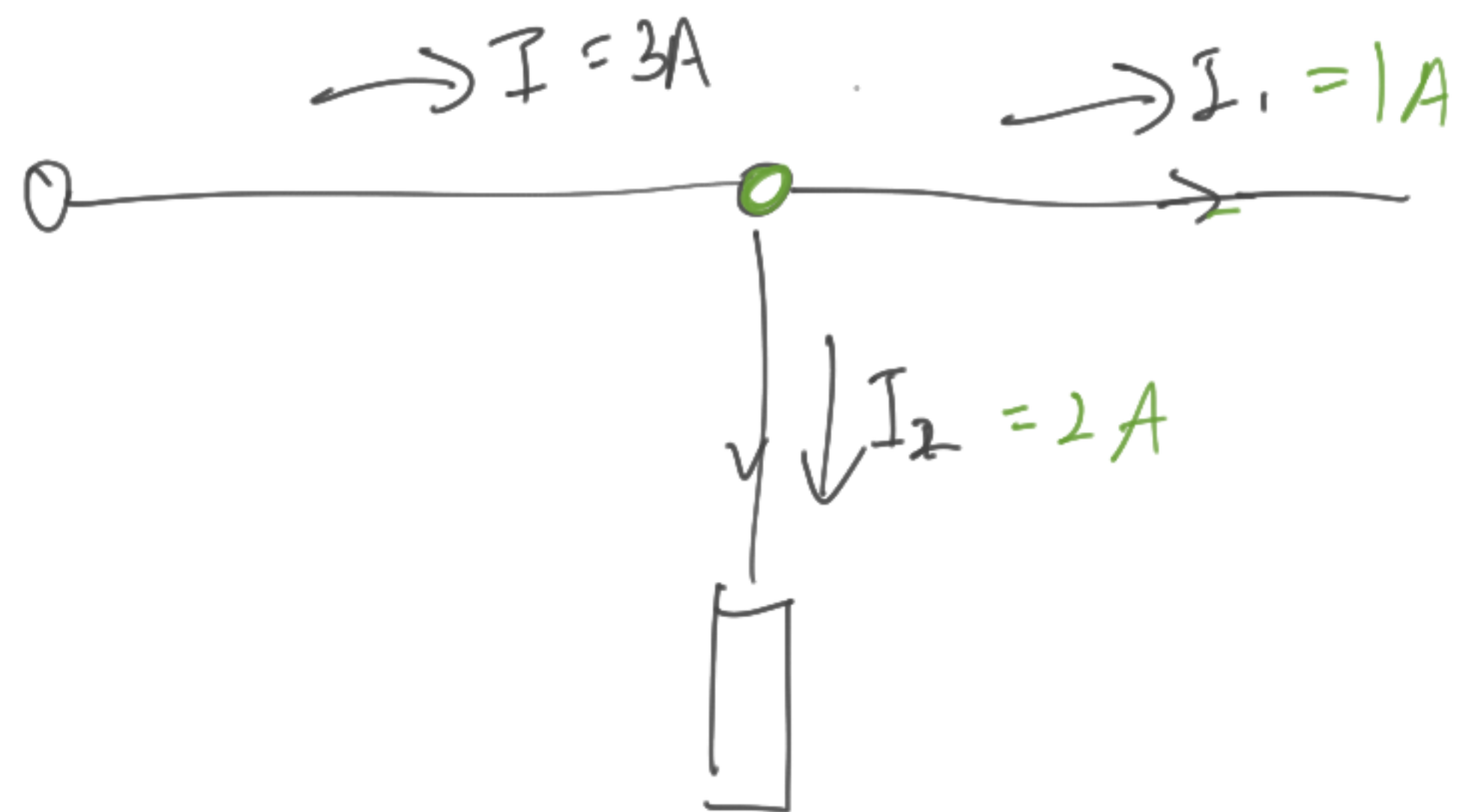

Current law
 $I_2 + I_1 = I = 3A$


Other funny

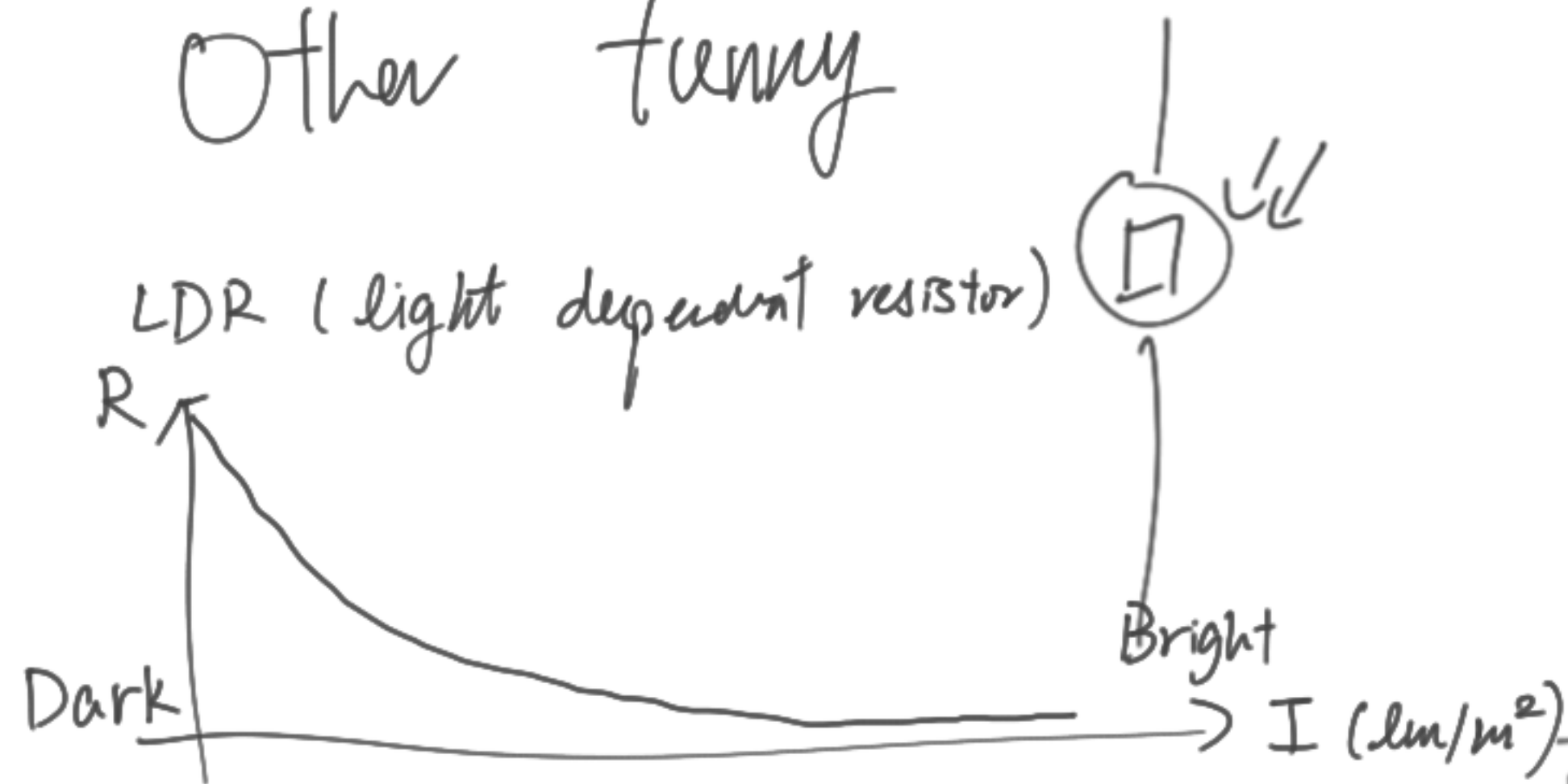

$$V_{R1} = 10 - 6 = 4V$$

$$V_0 - (V_{R1} + V_{R2}) = 0$$

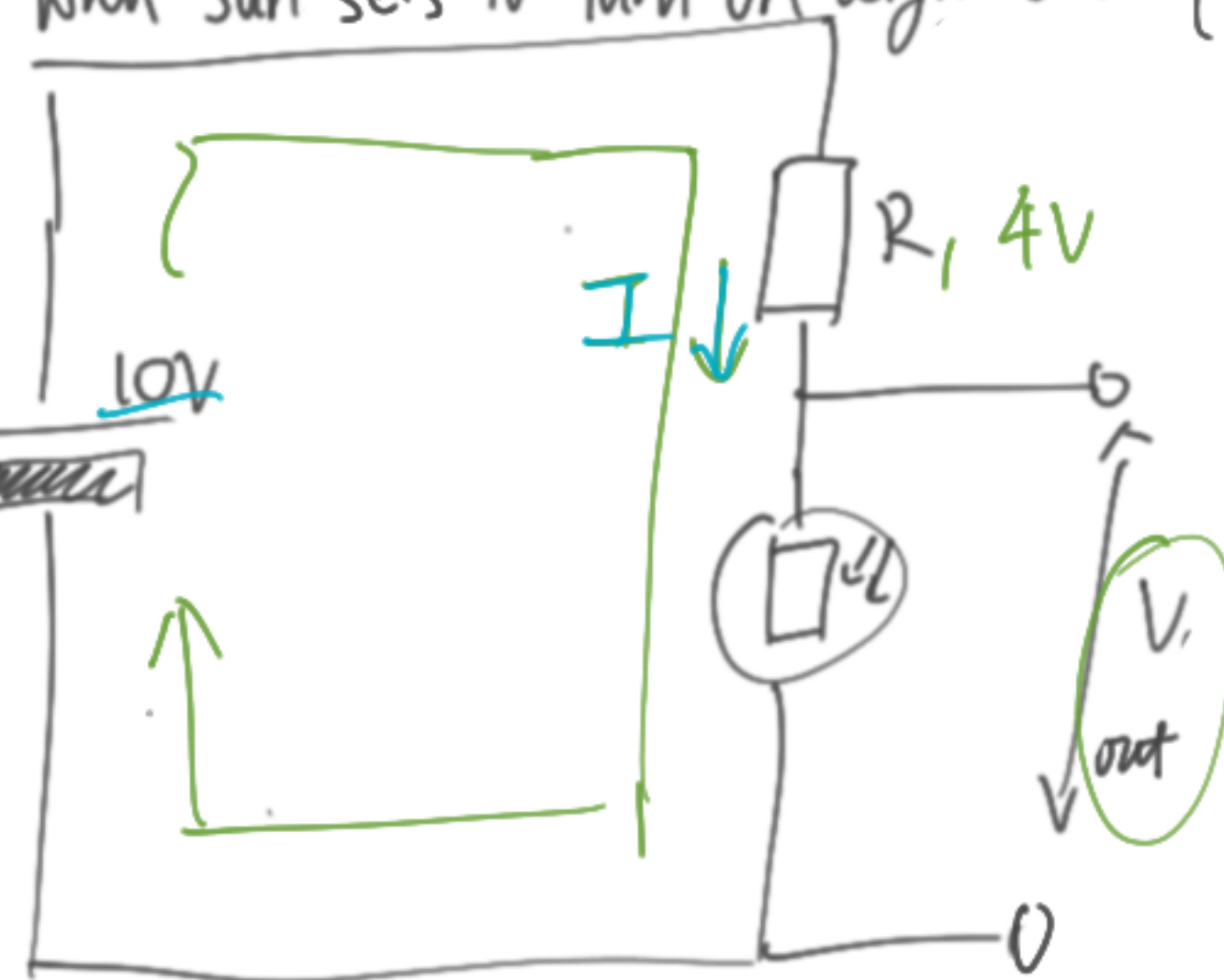Street lamp: Given R when sunset $= 500 \Omega$
 find suitable R_1 such that $V_{out} = 6V$
 when sun sets to turn on light bulb. (in ext circuit)



$$V_{R1} = I \cdot R_1$$

$$V_{R2} = 6V = I(500)$$

$$I = \frac{6}{500}$$

Thermistor

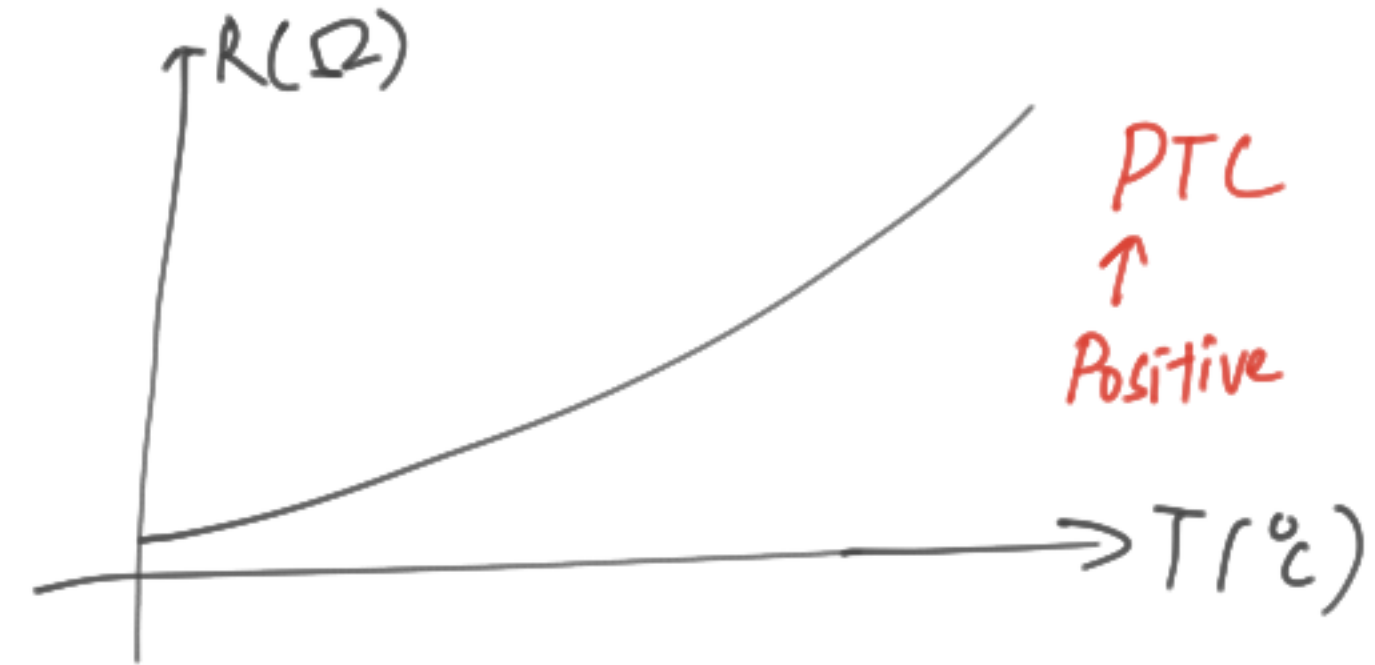
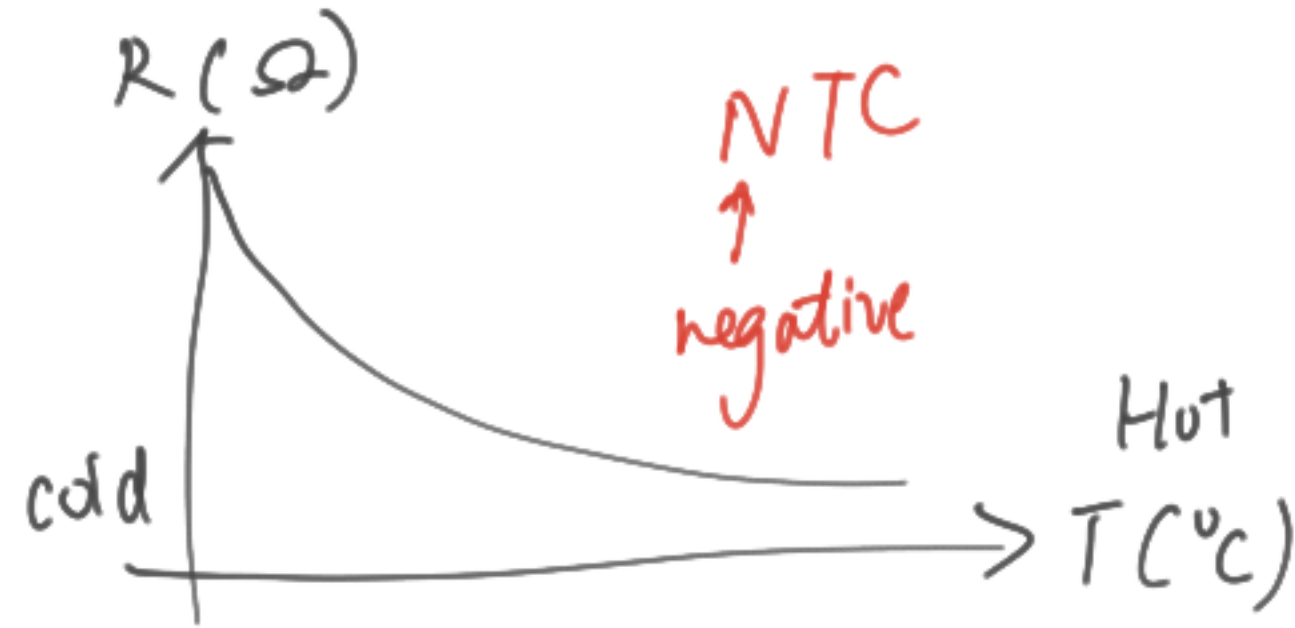


Figure 1 shows a circuit including a thermistor **T** in series with a variable resistor **R**. The battery has negligible internal resistance.

The resistance–temperature ($R-\theta$) characteristic for **T** is shown in **Figure 2**.

Figure 1


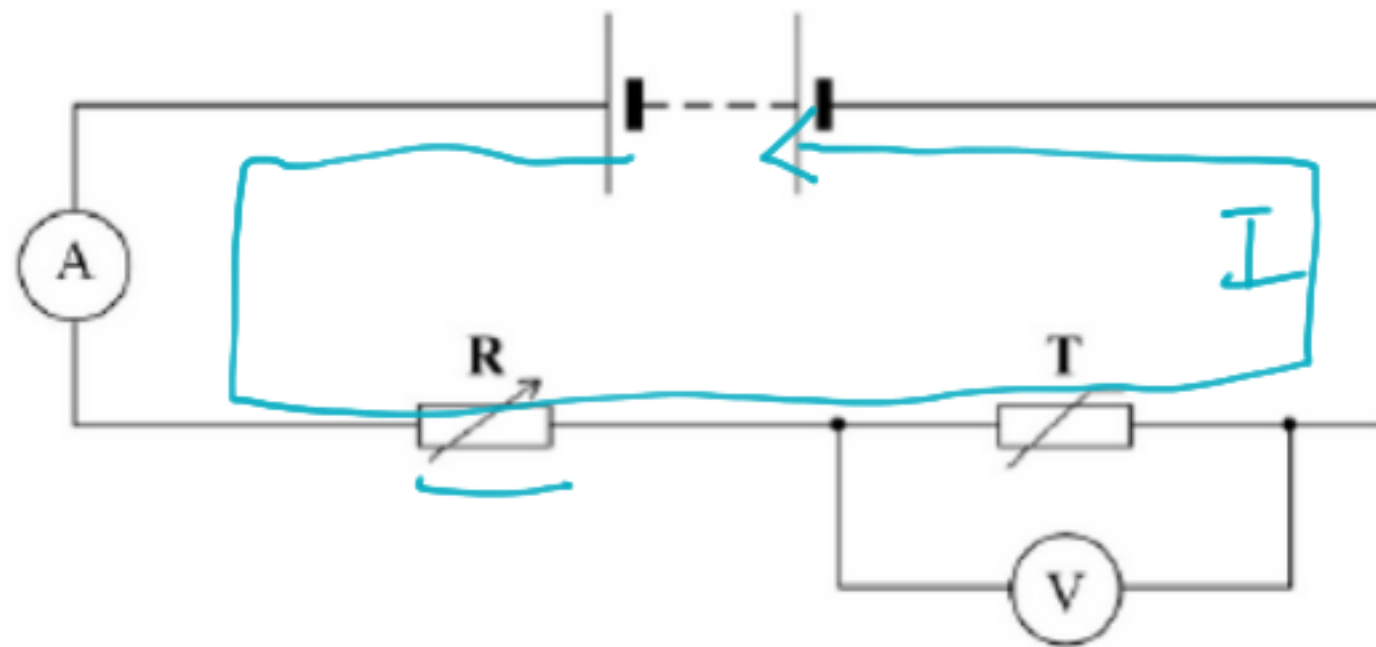


Figure 2

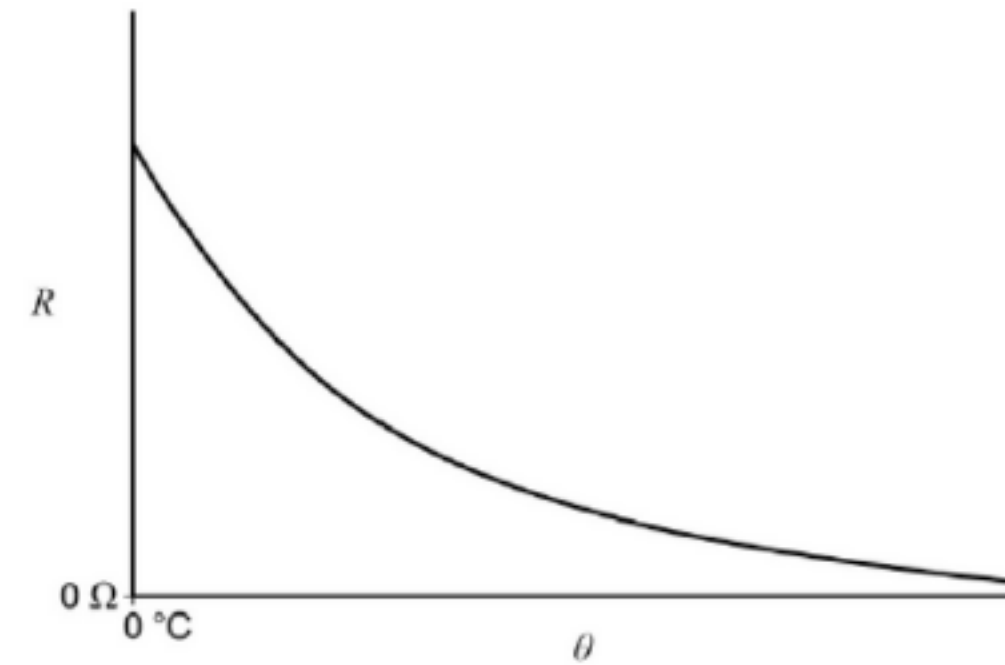

- (a) The resistor and thermistor in **Figure 1** make up a potential divider.

Explain what is meant by a potential divider.

Voltage in circuit is split up / divided by resistors connected in series

- (b) State and explain what happens to the voltmeter reading when the resistance of **R** is increased while the temperature is kept constant.

$$V_0 - V_R - V_T = 0 \Rightarrow V_0 - IR - IT = 0$$

$$I = \frac{V_0}{R+T}$$

$$V_T = IT = \frac{V_0 T}{R+T}$$

$$\rightarrow R \uparrow \Rightarrow I \downarrow \Rightarrow V_T = IT \Rightarrow V_T \downarrow$$

- (c) State and explain what happens to the ammeter reading when the temperature of the thermistor increases.

$$R_T \downarrow$$

$$As \quad I = \frac{V_0}{R+T}$$

when T increase, $R_T \downarrow$
therefore $I \uparrow$ (A) \uparrow

// V



- (d) The battery has an emf of 12.0 V. At a temperature of 0 °C the resistance of the thermistor is $2.5 \times 10^3 \Omega$.

The voltmeter is replaced by an alarm that sounds when the voltage across it exceeds 3.0 V.

Calculate the resistance of R that would cause the alarm to sound when the temperature of the thermistor is lowered to 0 °C.


$$V_R = 12 - 3 = 9V$$

$$V_R = 9 = 3 \cdot V_T$$

$$R = 3 (R_T)$$



resistance = 7500 Ω

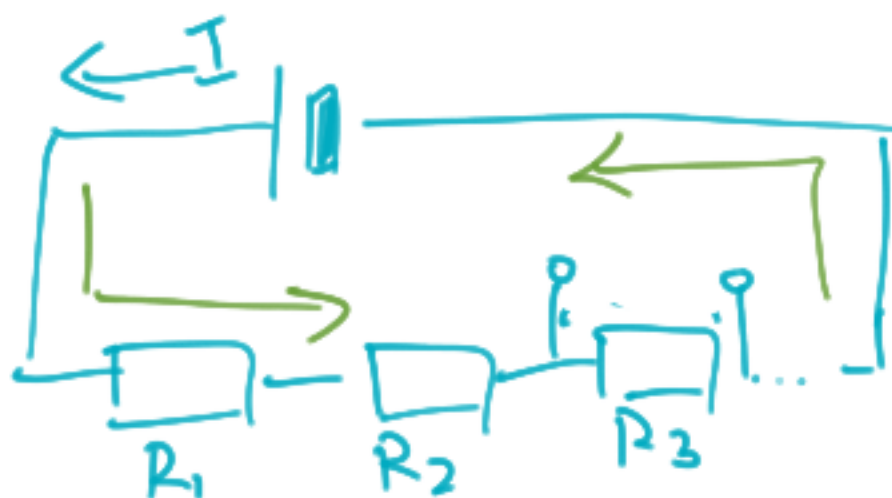

$$V = V_1 + V_2 + \dots = 0$$

$$V_i = I \cdot R_i$$

$$V_i = \frac{V_0}{\sum R} R_i$$

- (e) State **one** change that you would make to the circuit so that instead of the alarm coming on when the temperature falls, it comes on when the temperature rises above a certain value.

.....

.....

.....

(1)
(Total 9 marks)

(2)

$$V_1 + V_2 + \dots = V_0$$

$$I (R_1 + R_2 + \dots) = V_0$$

$$I = \frac{V_0}{\sum R}$$

8.

Figure 8.1

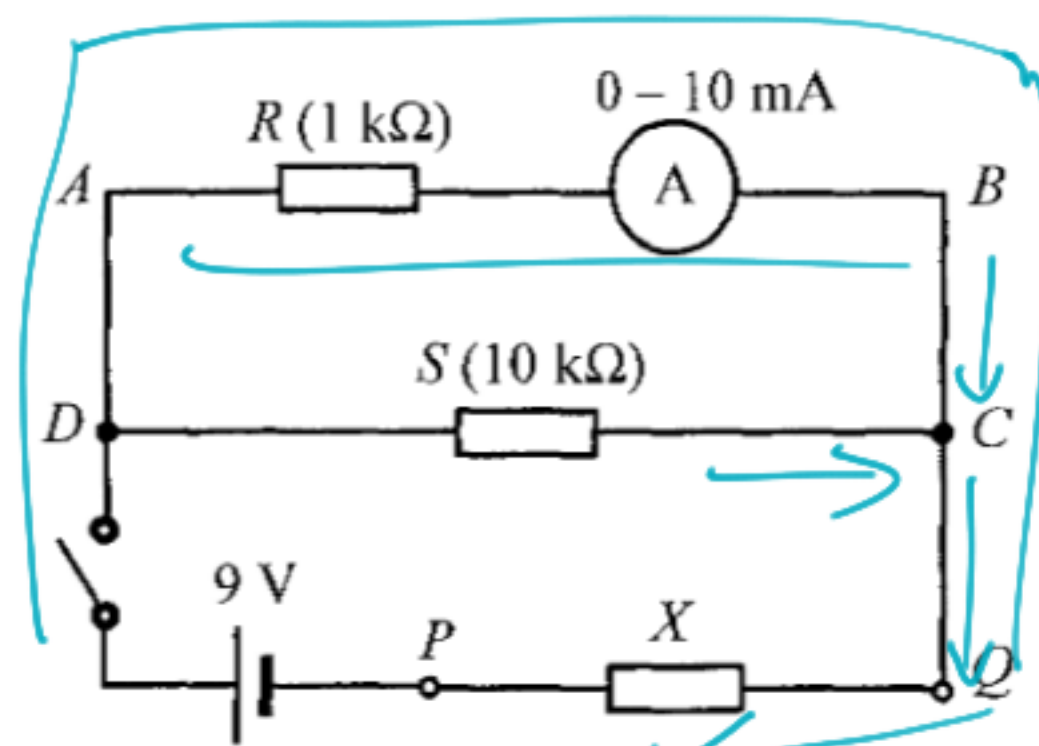


Figure 8.1 shows a circuit for measuring the resistance of resistor X connected across P and Q . The resistance of resistor S is $10\text{ k}\Omega$. The internal resistance of the 9 V cell and that of the ammeter are negligible.

(a) When the switch is closed, the ammeter reads 8.5 mA .

(i) What is the p.d. between A and B ?

(2 marks)

$$V_{AB} = IR$$

$$= 8.5\text{ V}$$

(ii) Find the current passing through resistor S .

(2 marks)

$$I_{AB} \cdot R_r = I_{DC} \cdot R_s$$

$$R_s = 0.0085\text{ mA}$$

(iii) Indicate on Figure 8.1 the direction of current in each of the three branches via C .

(iv) Deduce the p.d. across resistor X . Hence, find the resistance of X .

$$V_0 - V_s - V_x = 0$$

$$V_x = 0.5\text{ V}$$

$$I_x = 8.5 \times 10^{-4} + 8.5 \times 10^{-3}$$

$$I_x = 9.35 \times 10^{-3}\text{ A}$$

$$R_x = \frac{V_x}{I_x} \approx 53.5\text{ }\Omega$$

(b) State the purpose of connecting resistor R in series with the ammeter.

$$I = \frac{V}{R} \quad R \rightarrow 0 \quad I \rightarrow \infty$$

To prevent an excessive current from flowing through the ammeter, which may damage circuit components.