

Voltage and circuit

Sunday, 26 January 2025 9:08 AM

- Voltage
- Circuit
- The whole M

Voltage




Work done

$$W = Fd \cos \theta$$

$$dW = Fds \cos \theta$$



Electrical potential energy

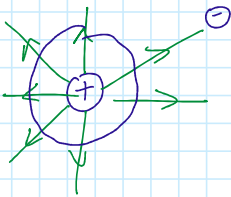

$$W = Fd \cos \theta$$

$$W = Fd$$

$$dW = Fds$$

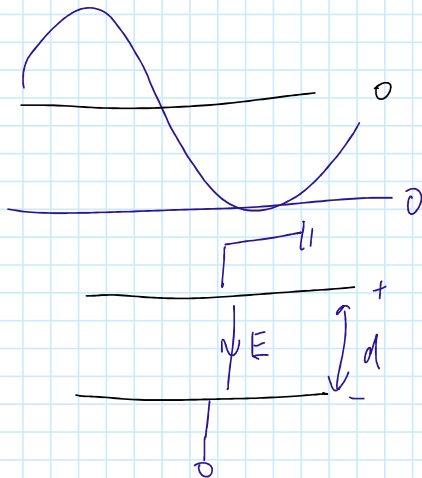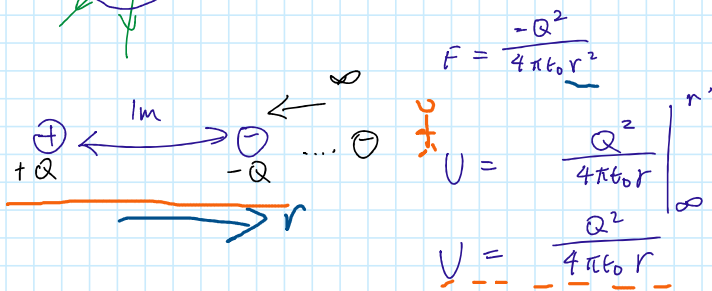

$$\frac{U(J)}{Q(C)} = V$$


$$V = \frac{Q}{4\pi\epsilon_0 r} \quad (\text{due to a pt charge})$$

$$V = \int E dl$$

$$V = -Ed$$

$$\Delta V = \Delta E$$


Wheatstone bridge

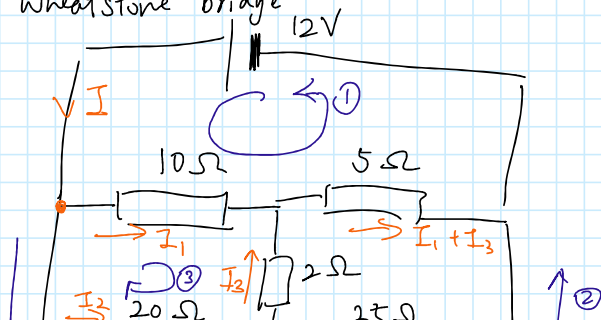

Circuit



- Kirchhoff law.

① Current law (conservation of charge)

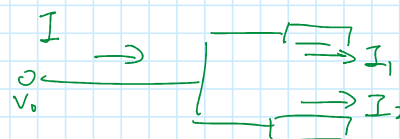

$$I = I_1 + I_2$$
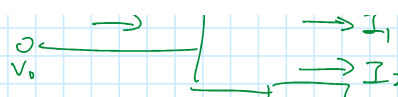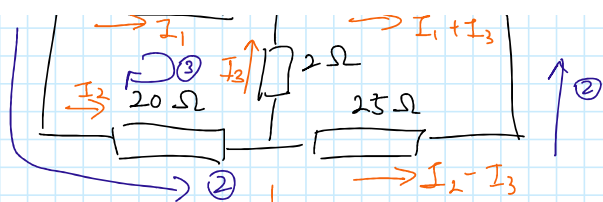
$$I_{\text{going in}} = I_{\text{going out}}$$



$$I = I_1 + I_2$$



$$I_{\text{going in}} = I_{\text{going out}}$$

② Loop rule

(conservation of energy)

$$\sum V = 0$$

$$\textcircled{1}: V - IR = 0$$

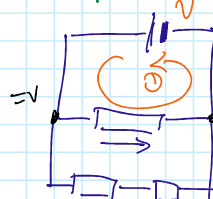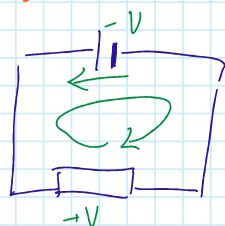

$$\textcircled{1} \quad 12 - 10I_1 - 5(I_1 + I_3) = 0$$

$$\Downarrow$$

$$15I_1 + 5I_3 = 12$$

$$\textcircled{2} \quad 12 - 20I_2 - 25(I_2 - I_3) = 0$$

$$45I_2 - 25I_3 = 12$$

$$\textcircled{3} \quad -10I_1 + 20I_2 + 2I_3 = 0$$

$$-5I_1 + 10I_2 + I_3 = 0$$

$$\boxed{I_3 = 5I_1 - 10I_2}$$

$$15I_1 + 25I_1 - 50I_2 = 12$$

$$40I_1 - 50I_2 = 12$$

$$45I_2 - 25(5I_1 - 10I_2) = 12$$

$$-125I_1 + 295I_2 = 12$$

$$40I_1 - 50I_2 = -125I_1 + 295I_2$$

$$165I_1 = 345I_2$$

$$I_1 = \frac{23}{11} I_2$$

$$40 \cdot \frac{23}{11} I_2 - 50I_2 = 12$$

$$I_2 = 0.357 \text{ A} \quad \left(\frac{66}{185} \right)$$

$$I_1 = 0.746 \text{ A} \quad \left(\frac{138}{185} \text{ A} \right)$$



$$I_3 = 5I_1 - 10I_2$$

$$= 0.162 \text{ A} \quad \left(\frac{6}{37} \text{ A} \right)$$

2 Battery

2 Battery

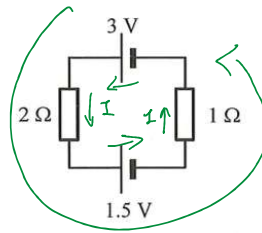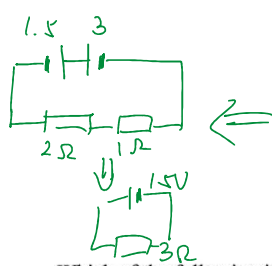25. Two cells of negligible internal resistance are connected to two resistors as shown.




$$\begin{aligned}
 +3 - 2I - 1.5 - I &= 0 \\
 1.5 - 3I &= 0 \\
 I &= 0.5 \text{ A}
 \end{aligned}$$

Which of the following is correct ?

| | direction of current | current in the circuit |
|----|----------------------|------------------------|
| A. | anticlockwise | 0.5 A |
| B. | clockwise | 0.5 A |
| C. | anticlockwise | 1.5 A |
| D. | clockwise | 1.5 A |


Batteries in parallel

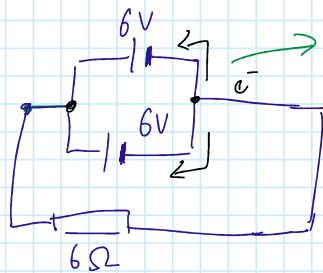

Total Voltage = 6V

$$\begin{aligned}
 (6)I &= 6 \text{ (V)} \\
 I &= 1 \text{ A}
 \end{aligned}$$

Charging

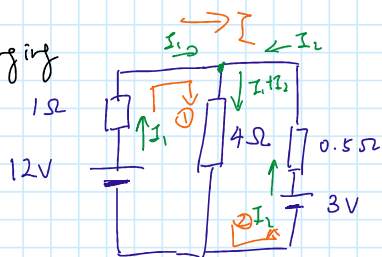

$$\textcircled{1} : I_1 + 4(I_1 + I_2) = 12$$

$$\textcircled{2} : 0.5(I_2) + 4(I_1 + I_2) = 3$$

$$\textcircled{3} : 5I_1 + 4I_2 = 12$$

$$\textcircled{4} : 4I_1 + 4.5I_2 = 3$$

$$\textcircled{3} - \frac{5}{4} \times \textcircled{4}$$


$$-\frac{13}{8} I_2 = \frac{33}{4}$$

$$I_2 = -\frac{66}{13} \text{ A}$$

$$= -5.08 \text{ A}$$

$$I_1 = \cancel{3.4 \text{ A}} \quad \cancel{1.5 \text{ A}} \\ 6.46 \text{ A}$$

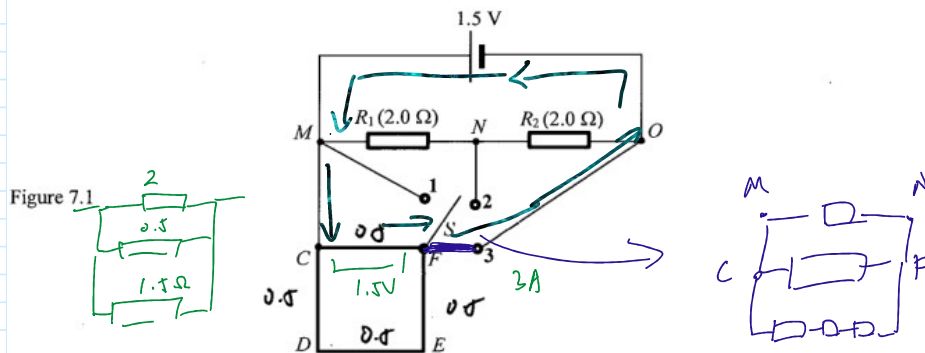- (b) Four such metallic wires in (a) are joined together to form a square coil $CDEF$. The coil is connected to a circuit consisting of a 1.5 V cell of negligible internal resistance and two identical resistors R_1 and R_2 , each of $2.0\ \Omega$, as shown in Figure 7.1.



- (i) To which terminal (1, 2 or 3) should switch S be connected in order to have a maximum current flowing through side CF of the coil? (1 mark)


Terminal 3

- (ii) With S connected to terminal 2, find the equivalent resistance across MN . (2 marks)

$$R_{eq} = \frac{1}{\frac{1}{2} + \frac{1}{2}} = 1\ \Omega$$

Magnetic forces

①: On a moving charge

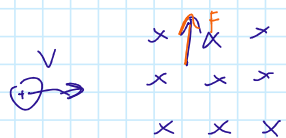


$$\vec{F} = q \vec{v} \times \vec{B}$$

$$dW = \vec{F} \cdot \vec{v} dt = 0$$

② Force on a current.

$$\vec{F} = I \vec{L} \times \vec{B}$$

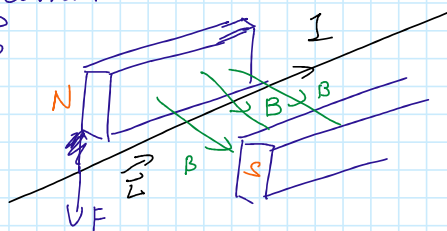

$$\vec{\tau} = \vec{r} \times \vec{F}$$

